



HAM TIPS

PUBLISHED - IN - THE - INTEREST - OF - RADIO - AMATEURS - AND - EXPERIMENTERS

VOLUME IX, No. 2

EDITORIAL OFFICES, RCA, HARRISON, N. J.

MAY, 1949

"TINY TRAN" - A MINIATURE RIG FOR 10 AND 11 METERS MOBILE TRANSMITTER DESIGNED AROUND NEW RCA-5763 PENTODE

By
MARTIN GASPIERIK, W2NEU
and
PAT PATTERSON, W2VBL
RCA Tube Department

FREQUENCY MULTIPLIER



Requiring only one ganged-tuning control, the all band frequency multiplier makes shifting from one band to another a simple operation. Its design provides compactness and good shielding to minimize TVI.

ALL BAND FREQUENCY MULTIPLIER IS GANGED TUNED FOR RAPID QSY

By
GEORGE D. HANCHETT, JR., W2YM
RCA Tube Department

The increasing popularity of 80-meter VFO's has stimulated the need for a companion unit, a frequency multiplier, which can be used with the VFO to operate on all the lower frequency bands: 80, 40, 20, 15, and 10-11 meters. Such a unit, designed to work with the VFO described in the last issue of HAM TIPS,[†] is the subject of this article. Its design, in addition to providing the usual desirable qualities of simplicity and compactness, features good shielding for a minimum of TVI.

Because the multiplier requires only one ganged tuning control, shifting from one band to another is a very simple operation. Although a preliminary design of this multiplier employed broad-band tuned circuits in order to eliminate the one tuning control, tests indicated that the broad-tuned arrangement was more likely to cause TVI than the ganged-tuned circuit.

The circuit itself is conventional. Four stages are used; a 7-megacycle doubler, a 14-megacycle doubler, a 28-megacycle doubler, and a 21-megacycle tripler.

Construction Details

An aluminum chassis 3" x 4" x 17" is used for the multiplier. All the components with the exception of the tubes and heater transformer are mounted inside the chassis. An aluminum panel, 5 1/4 inches wide,

covers the open side of the chassis and serves as the front panel. The metal type RCA-6L6 was selected for all stages because its metal shell provides complete shielding of the tube. Another tube type could have been used with equally satisfactory results, but since it was desired to operate the multiplier from a single 350-volt supply and to obtain enough power to excite an RCA-813 as a final amplifier, the 6L6 was chosen.

The four series tracking capacitors (C_1 , C_2 , C_3 , and C_4) are mounted on the top side of the chassis between the tank coils. The parallel padding capacitors (C_5 , C_6 , C_7 , C_8 , and C_9) are mounted behind each section of the ganged tuning capacitors (C_1 , C_2 , C_3 , C_4 , and C_5) and are available from the bottom of the chassis. The tuning control for the ganged

(Continued on Page 3, Column 1)

Being avid mobile fans, originally by necessity, later by choice, the possibilities envisioned in the recently announced rf power pentode, the RCA-5763, were intriguing. The result was "Tiny-TRAN", a miniature mobile transmitter for 10 and 11 meters. This 5 x 9 1/2 x 2 1/2 inch rig operates with a plate input power to the final of 15 watts at 27 to 30 Mc. The heater drain is only 2.7 amperes at 6.0 volts and the plate supply 140 ma at 300 volts.

Let's take a look at the output tube first. The 5763 is a 9-pin miniature transmitting type, capable of 15 watts input up to 175 Mc. The high-perveance characteristic is particularly suitable for mobile operation because it considerably reduces power supply problems. Another important feature is the heater rating. The cathode is so constructed as to give full emission with only 6.0 volts applied to the heater. Heater voltage is an important consideration in mobile work since, more often than not, the battery voltage less the line drop approximates this 6-volt figure.

Quite naturally, its size, too, is interesting, since the 5763 is only slightly larger in diameter than the


7-pin miniature 6AQ5. When the 5763 is used in the rf stages, and other miniatures are used in the audio stages, economy of space is at a maximum.

The heater requirements and maximum ratings of the RCA-5763 are as follows:


Heater Voltage (ac or dc)	6.0 \pm 10% volts
Heater Current	0.75 ampere
DC Plate Voltage	300 max. volts
DC Grid-No. 3 (Suppressor)	
Voltage	0 max. volts
DC Grid-No. 2 (Screen)	
Voltage	250 max. volts
DC Grid-No. 1 (Control-Grid)	
Voltage	125 max. volts
DC Plate Current	50 max. ma
DC Grid-No. 2 Current	15 max. ma
DC Grid-No. 1 Current	5 max. ma
Plate Input	15 max. watts
Grid-No. 2 Input	2 max. watts
Plate Dissipation	12 max. watts

(Continued on Page 3, Column 1)

THE "TINY-TRAN"

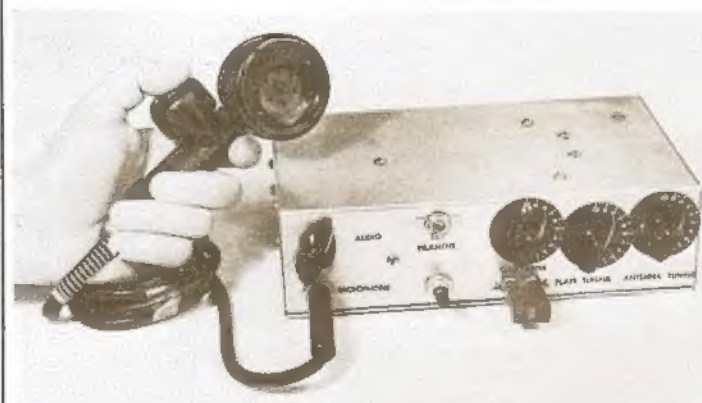

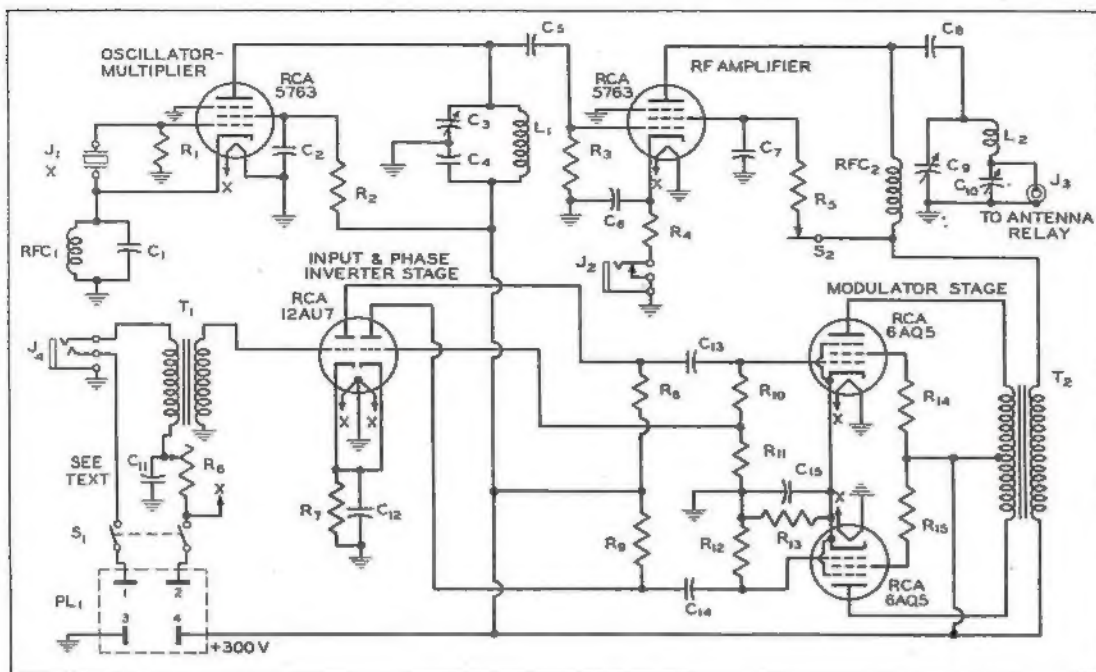Completely housed in a 5" x 9 1/2" x 2 1/2" chassis, this miniature transmitter is particularly suited for mobile work. It uses the new RCA-5763 rf power pentode as an output tube, and operates with a plate input power to the final of 15 watts at 27 to 30 Mc.



Schematic of the "Tiny-Tran"

"TINY TRAN"

(Continued from Page 1, Column 4)

Design Considerations

Because mobile operation can take place anywhere, it seemed advisable to design a unit readily adaptable to a Crosley or a Cadillac, a Piper Cub or a DC-6, a rowboat or the Queen Mary. By employing miniature tubes and small components, it was possible to place the entire circuit inside a small metal chassis $5 \times 9\frac{1}{2} \times 2\frac{1}{2}$ inches. This size and shape lends itself readily to mounting in any number of positions about the panel of a car. Even the glove compartment of most models will accommodate such a box. All controls are brought to the front panel with the exception of the meter jack, which is brought out in the rear.

The bottom plate of the chassis becomes the side panel, and gives access to the "innards" of the rig by removal of the self-tapping screws. Two sub panels are cut to fit as indicated in the photographs. The lower panel holds the audio stages, while the upper one supports the rf unit. Some of the components are mounted directly on the chassis, but, despite cramped quarters, all parts and wiring are quite accessible.

Because the 5763 is designed to operate at a high temperature (maximum 250°C) and requires good ventilation, a series of holes is drilled in the top of the case and in the cover plate directly opposite the tubes. A similar arrangement is also made for cooling the modulator stage.

RF Section

The rf section utilizes two of the new RCA-5763's, one as triode oscillator-multiplier, and the other as an rf final amplifier. When a crystal in the order of 7 Mc is used,

ample drive to the grid of the final at 28 Mc is obtained readily.

An important space-saving feature is the triode coil which is a commercial rf choke, the size of a one-watt resistor. The inductance and Q requirements of this coil are met very satisfactorily by the Ohmite Choke, Z144.

The antenna coupling system is especially interesting because it very effectively discriminates against harmonics. (1) This type of coupling (a modified pi network) compared to the conventional link coupling, provides only $\frac{1}{4}$ of the 2nd-harmonic output, $\frac{1}{9}$ of the 3rd-harmonic output, and proportionately smaller amounts of higher-order harmonics. Maximum loading is obtained by tuning the capacitors in the pi network. In one particular installation of this "Tiny-Tran", the antenna was fed with a 2-foot length

of 72-ohm coax line. Placement of the transmitter in the front area of the car, incidentally, allows use of a standard 4-section collapsible receiving antenna capable of being extended to 100 inches or more. This position eliminates the need for drilling holes in the rear deck of the car for the more costly police-type whips.

Audio Section

The audio section is also simple in design. An RCA 12AU7 medium-mu twin triode is used as the input phase-inverter stage, and is coupled by means of capacitors to a pair of 6AQ5's which function as class AB modulators. All operating conditions are carefully chosen so that clean, crisp speech results. This tube line-up, as in the rf section, allows either a parallel or series-parallel heater connection for 6-or

12-volt battery operation. (Most personal aircraft and some small cars use 12-volt electrical systems).

The miniature components given in the parts list are the ones used in this transmitter. Substitutions may be made if they are equivalent in size as well as electrical characteristics.

The antenna transfer relay is mounted at the base of the antenna and is controlled by the circuit that operates the dynamotor relay. Thus, when the microphone push-to-talk switch is pressed, the dynamotor is started, the antenna transferred, and voltage applied to the mike button.

Construction

The chassis, the two shelves, and the cover plate are first drilled and shaped. Next the shelves and major components are mounted inside the chassis to check their fit. The only component which requires any change in adjustments to insure a proper fit is the modulation transformer. Its rear mounting ear is bent down even with the side of the transformer shell, thus making the unit fit snugly against the rear wall of the chassis to which the transformer is bolted.

After all components fit satisfactorily, the rf and modulator shelves are removed and wiring of the transmitter started. The two shelves should be wired as completely as possible before mounting them inside the chassis. Leads leaving the shelves for connection to other components should be left sufficiently long for easy connection. The rf shelf, which contains the 5763 oscillator at the left and the 5763 amplifier at the right, should be mounted in the chassis first. Wiring for the rf section of the transmitter can then be completed. The hot heater supply lead for this section goes directly up from the main switch, S1. The B+ supply lead goes to a 2-terminal lug strip mounted below the shelf on the mounting screw of an rf amplifier socket. The B+ end of RFC2 is secured to a 1-terminal lug strip mounted to the right of the rf amplifier tube above the shelf. This lead is covered with a varnished cambric tubing and passed through a small hole in the rf shelf in such a manner as to bring the plate lead directly away from the grid connection. The B+ end of L1 is also connected to a 1-terminal lug strip. All leads are kept short and a common ground point is used for each stage.


Checking The RF Section

It is suggested that the rf section be tested before mounting the audio shelf in the chassis.


For preliminary testing in the ham shack a half-wave dipole cut to frequency and center fed with a section of 72-ohm coax approximately equal in length to that used in the mobile installation should be used. Crystals between 7.125 Mc and 7.425 Mc should be used for 10-meter phone and between 6.79 Mc and 6.857 Mc for 11 meters. In-

(Continued on Page 3, Column 2)

A REAL HANDFUL

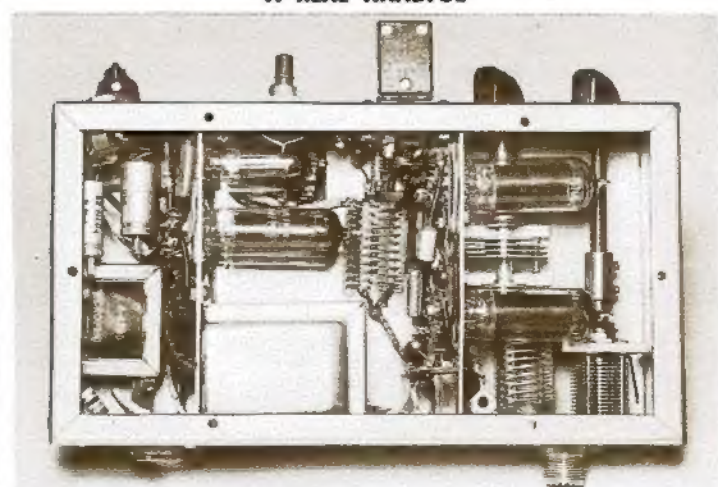

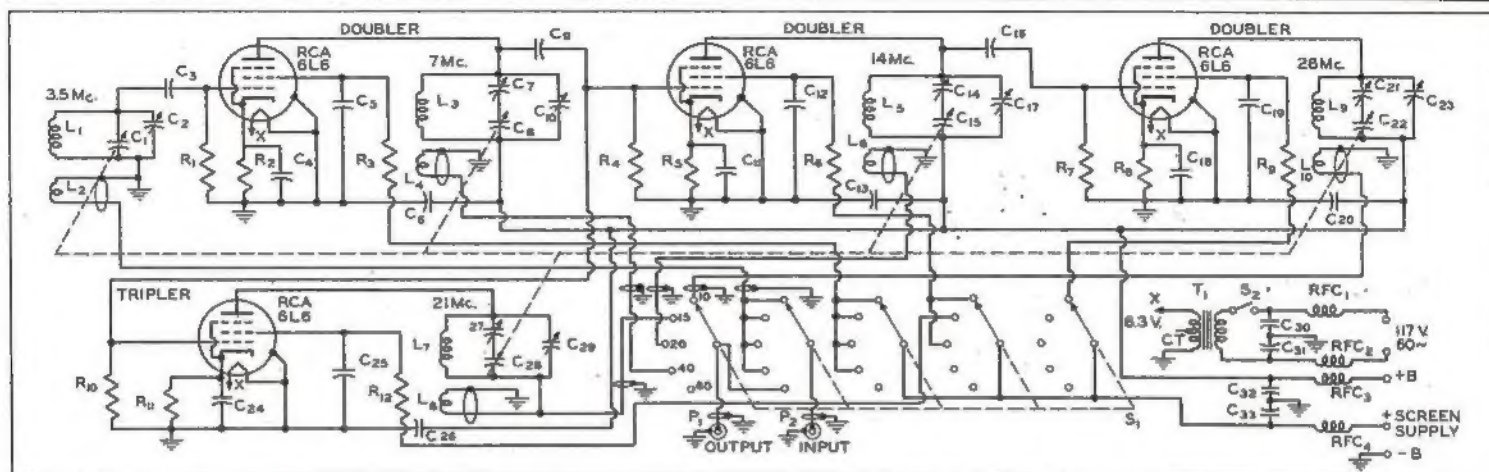An inside view of the miniature transmitter reveals two sub panels and the manner in which parts are positioned and wired. Despite cramped quarters, all components are fairly accessible.



Schematic of the gang-tuned frequency multiplier.

FREQUENCY MULTIPLIER

Continued from Page 3, Column 1

of the VFO to 3.4 megacycles. When the multiplier band switch is in the 3.5-megacycles (80-meter) position, output power is available at the coaxial output connector (P_1). Next, turn the band switch to the 7-megacycle (40-meter) position and apply heater voltage to the multiplier tubes. Connect a vacuum-tube voltmeter such as the VoltOhmyst* Electronic Meter WV-195-A to the grid terminal of the first (7-megacycle) doubler stage. Before the plate voltage is applied, set the ganged tuning

capacitors for maximum capacitance and adjust the parallel padding capacitor C_2 so that the input tank circuit is resonant. Resonance is indicated by maximum meter reading. If a low-range milliammeter is used, it should be connected in series with the grid resistor on the ground side. The excitation from the VFO should be increased until the voltmeter reads approximately 100 volts. If a milliammeter is used, the current should be approximately 3 ma. Now, turn the ganged tuning capacitors to the position of minimum capacitance and then reset the VFO frequency for maximum grid

voltage. The frequency of the VFO should be slightly above 3.75 megacycles.


In the alignment of all stages, the meter should be placed either across the grid resistor of the stage following the one being aligned or else across the cathode resistor of the stage being aligned. To adjust the 7-megacycle doubler stage, leave the VFO at 3.75 megacycles and the ganged tuning capacitor at minimum capacitance, and apply voltage to the plates and screens. As soon as this voltage is applied, adjust the parallel padding capacitor C_2 for resonance without delay. It is necessary to make this adjustment as

adjust the parallel padding capacitor C_{17} to restore resonance. Only a slight change should be necessary.

All the other multiplier stages are aligned in exactly the same manner. The cathode current of the stage being used to excite the driver or final may be increased to as much as 60 or 70 ma. Cathode currents of all other stages will run approximately 25 ma per stage. For direct excitation of a final 813 power amplifier, a cathode current of 50 ma for the driving stage was found to be more than sufficient.

*"Self-contained VFO Designed for Stability on All Bands", by Andrew Rau, Jr., W3KBZ, (Ham Tips, Jan. Feb. 1949)
*Registered Trade Mark, U.S. Pat. Office

INTERIOR VIEW OF MULTIPLIER

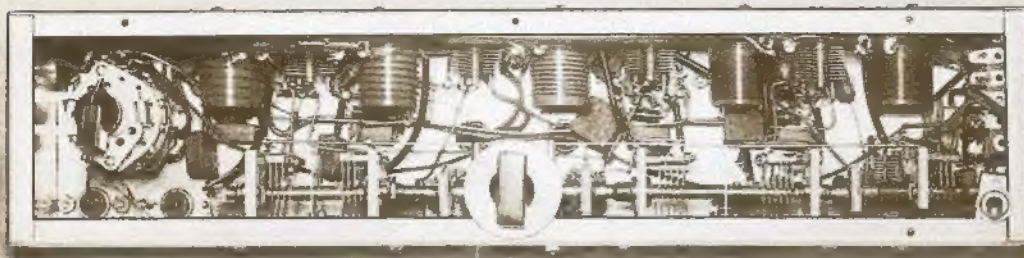

Well planned design of the frequency multiplier reveals simplicity of construction and the compact manner in which wiring and components are placed. The tuning control for the ganged tuning capacitors is brought out to the front panel by a right-angle drive shaft, shown in center of photo.

PARTS LIST

C_1	25 uuf, variable, Cardwell ZR-25-AS
C_2	100 uuf, variable (APC-100)
C_3	47 uuf, 500 V, mica
C_4, C_{11}, C_{15}	.01 uf, 300 V, mica
C_5, C_{12}, C_{16}	.0005 uf, 500 V, mica
C_6, C_{13}, C_{18}	.0003 uf, 500 V, mica
C_7, C_{14}, C_{19}	.0003 uf, 500 V, mica
C_8, C_{10}	75 uuf, variable (APC-75)
C_9, C_{17}	35 uuf, variable, one section of Cardwell ER-35-AD
C_{10}, C_{14}, C_{18}	22 uuf, 500 V, mica
C_{11}, C_{15}, C_{19}	50 uuf, variable (APC-50)
C_{12}, C_{16}, C_{17}	15 uuf, 500 V, mica
C_{13}, C_{18}, C_{19}	25 uuf, variable (APC-25)
C_{14}, C_{19}	25 uuf, variable, one section of Cardwell ER-25-AD
R_1, R_4, R_7	33,000 ohms, 1 watt, carbon
R_2, R_5, R_8	560 ohms, 1 watt, carbon
R_3, R_6, R_9	15,000 ohms, 2 watts, carbon
S_1	6 pole, 3 wafer, 6 position switch
S_2	SPST, 3 amp toggle switch
T_1	Heater transformer, 4.0 amps at 6.3 V
P_1, P_2	Coax male chassis connectors
$RFC_1, RFC_2, RFC_3, RFC_4$	#24 Enamelled wire, wound on 100,000 ohms, 2 watts, carbon resistor
L_1	35 turns #22, wound 1" on National XR-2 form
L_2	21 turns #20, wound 1" on National XR-2 form
L_3	13 turns #20, wound 1" on National XR-2 form
L_4	8 turns #20, wound 1" on National XR-2 form
L_5	6 turns #20, wound 1" on National XR-2 form
L_6, L_7, L_8	2 turns #18, wound close to cold end of tank coils

HAM TIPS is published by the RCA Tube Department, Harrison, N. J., and is made available to Amateurs and Radio Experimenters through RCA tube and parts distributors.
H. S. STAMM, W2WCT, Editor
JOHN L. REINARTZ, W3RB, Technical Adviser

quickly as possible because the out-of-resonance plate current may be excessive and damage the tube. The cathode current is approximately 25 ma; the cathode voltage as measured with the VoltOhmyst Electronic Meter is approximately 14 volts.

To complete the adjustment of the 7-megacycle doubler stage, tune the VFO to 3.4 megacycles and set the ganged tuning capacitor for maximum capacitance. Then, adjust the series padding capacitor (C_1) for maximum voltage across the grid resistor (R_1) of the 14-megacycle doubler stage. Return the VFO to 3.75 megacycles and